

Normally Closed Door Triggers

Some door triggers rest at ground when the doors are closed and create an open circuit when the doors are open. This makes interfacing with these vehicles more difficult to integrate and alarm or remote start into. This diagram will show you how to interface with these vehicles. All resistors are 10K Ω and all diodes are 1 amp.

